


# Instruction Set Architecture

- Instructions: Commands for basic operations
- Types and formats of instructions
- Addressing modes of instructions
- Machine codes of instructions
- Data representation
- Registers and uses
- Memory address

Computer Engineers/Hardware


Engineers must understand ISA to design/implement hardware details of a computer:

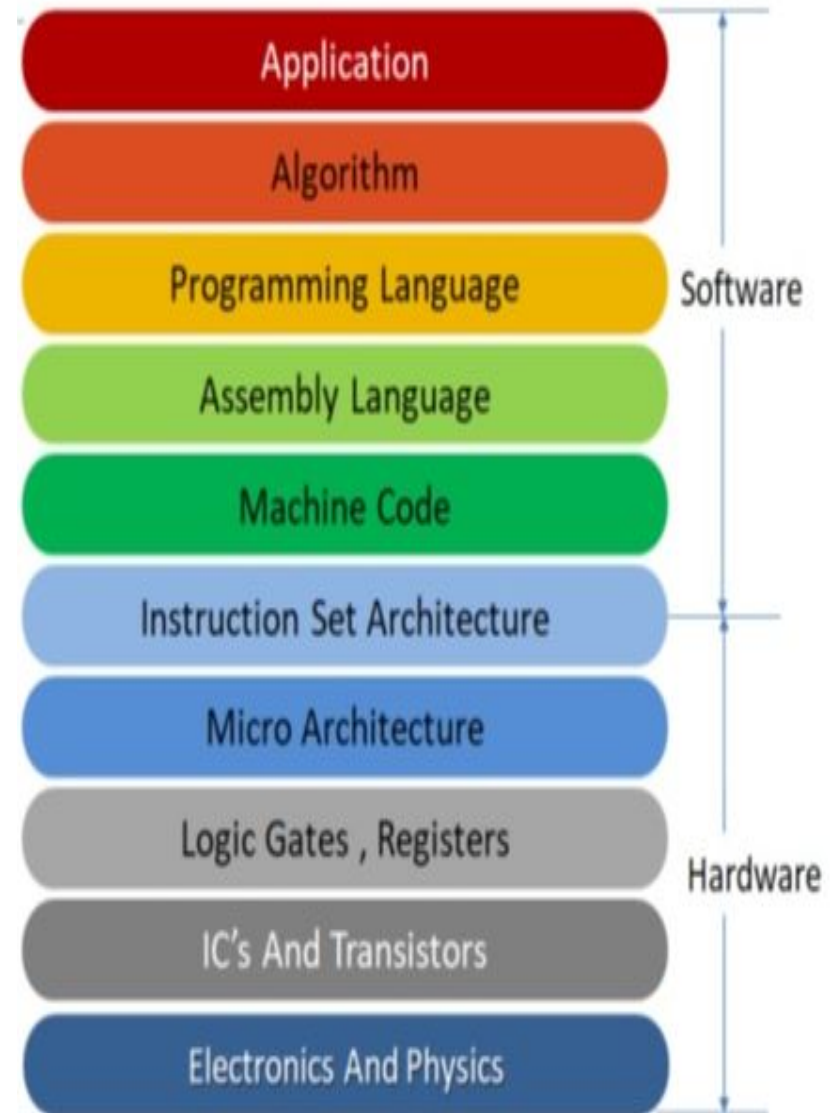Microarchitecture and it's design using ICs, logic gates and associated components.



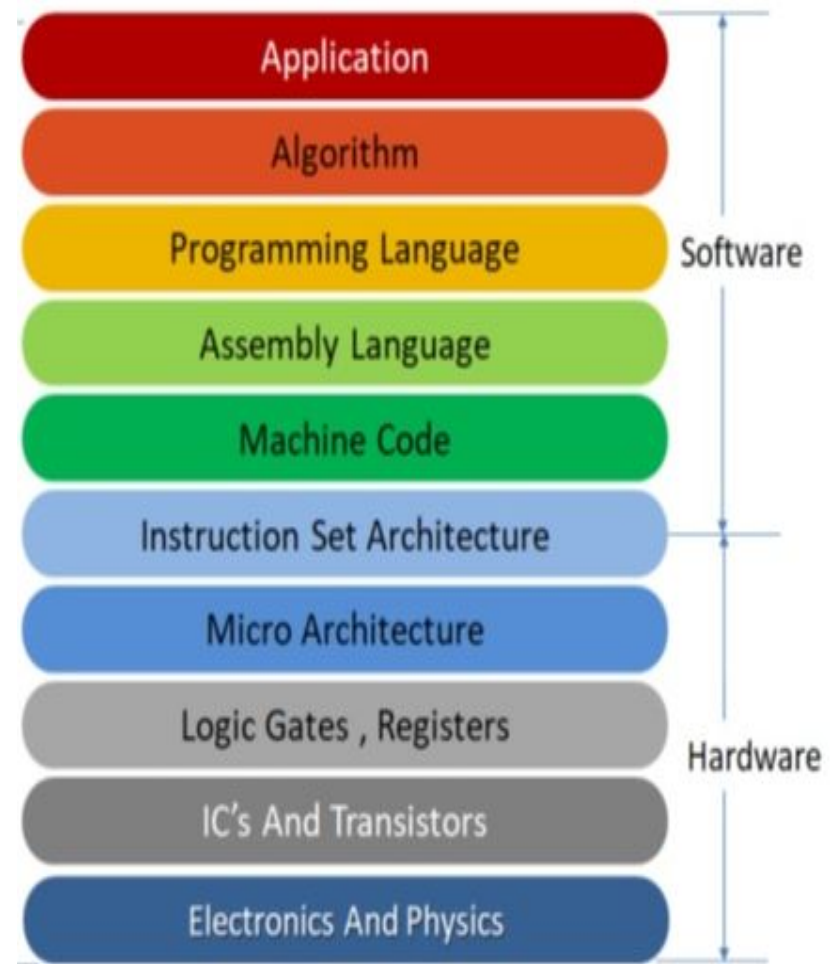
# Micro-architecture

- The level above the digital logic level is the **microarchitecture level**.
- Its job is to implement the ISA (Instruction Set Architecture) level above it,
- The design of the microarchitecture level depends on the ISA being implemented, as well as the cost and performance goals of the computer.
- Many modern ISAs, particularly RISC designs, have simple instructions that can usually be executed in a single clock cycle.
- More complex ISAs may require many cycles to execute a single instruction.
- Executing an instruction may require locating the operands in memory, reading them, and storing results back into memory.



# Microarchitecture: *Implementation of an ISA*

---

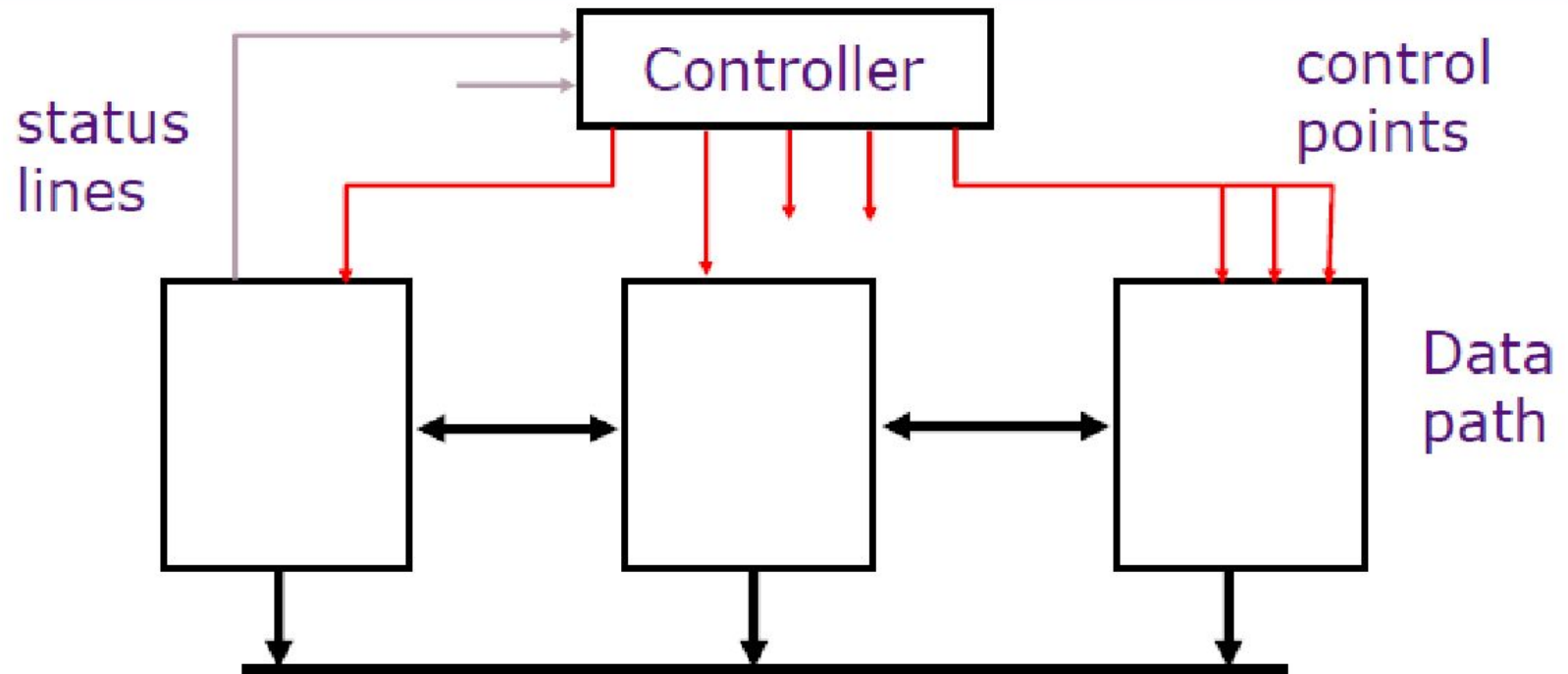

*Structure:* How components are connected.


*Static*

*Behavior:* How data moves between components

*Dynamic*

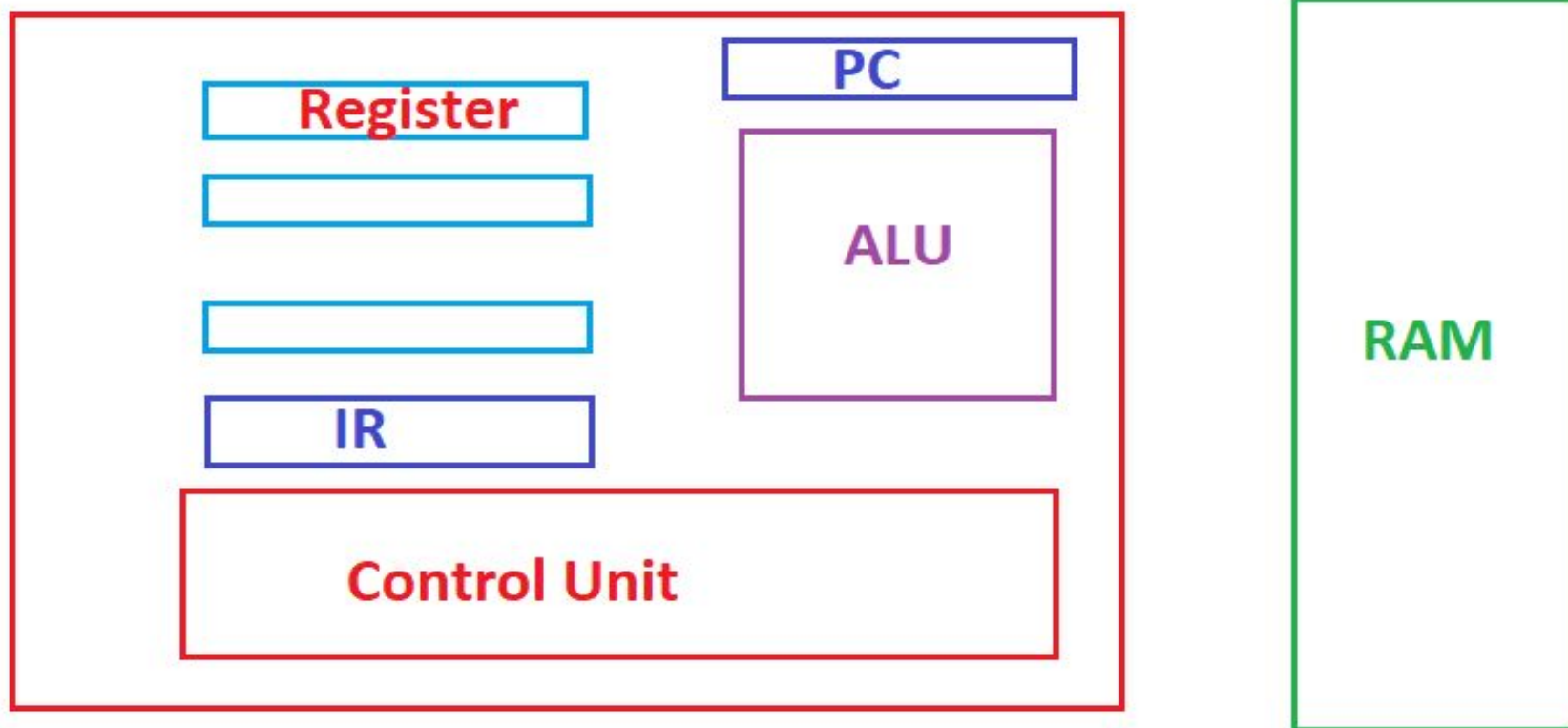
# Microarchitecture

- Design of Registers, ALU, Control Unit
- How to interconnect these and how to control/flow information among these
- How to select particular operation in ALU
- How to select particular registers (read/write)
- How to access memory (read/write)



 
# Hardware Elements

- Combinational circuits
  - Mux, Demux, Decoder, ALU, ...




 - Synchronous state elements
  - Flipflop, Register, Register file, SRAM, DRAM




*Edge-triggered: Data is sampled at the rising edge*

# Register Files

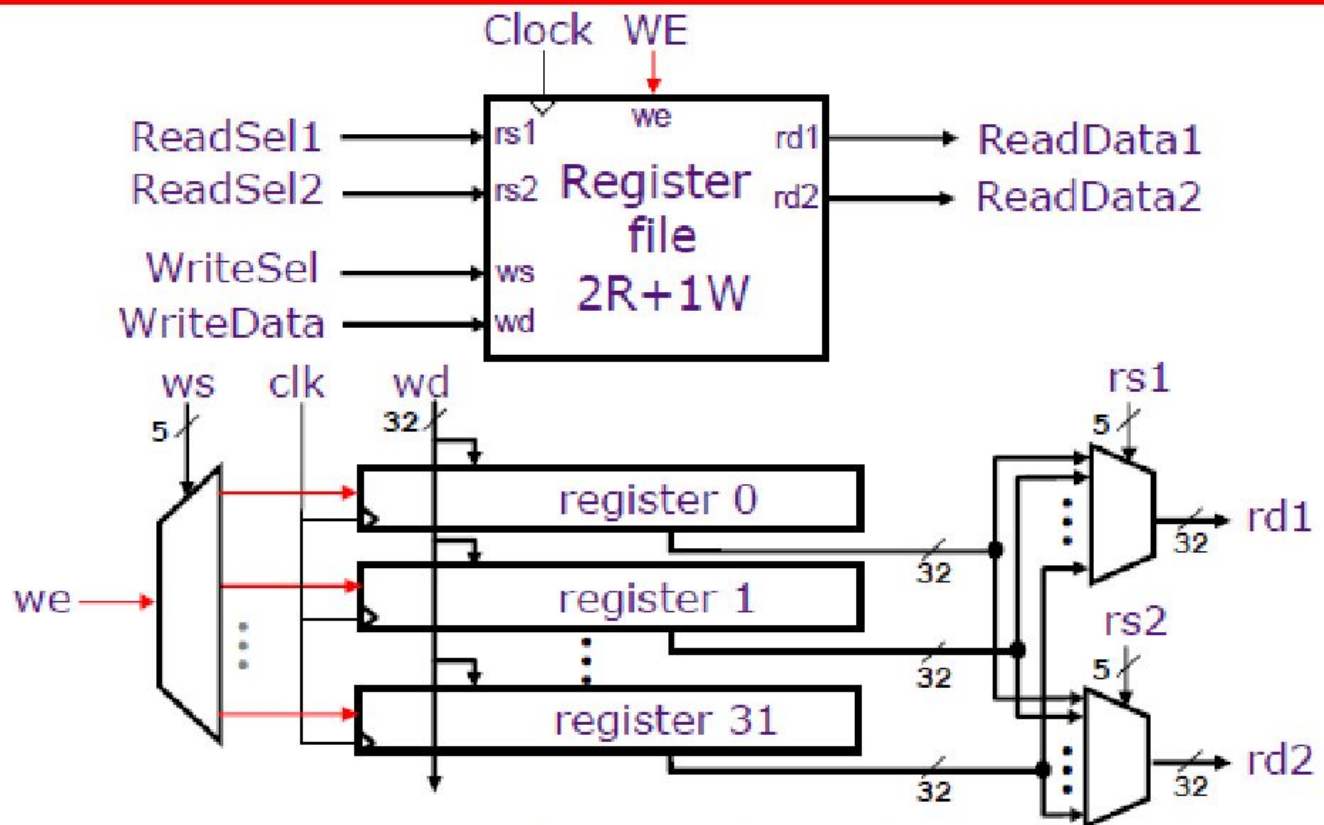

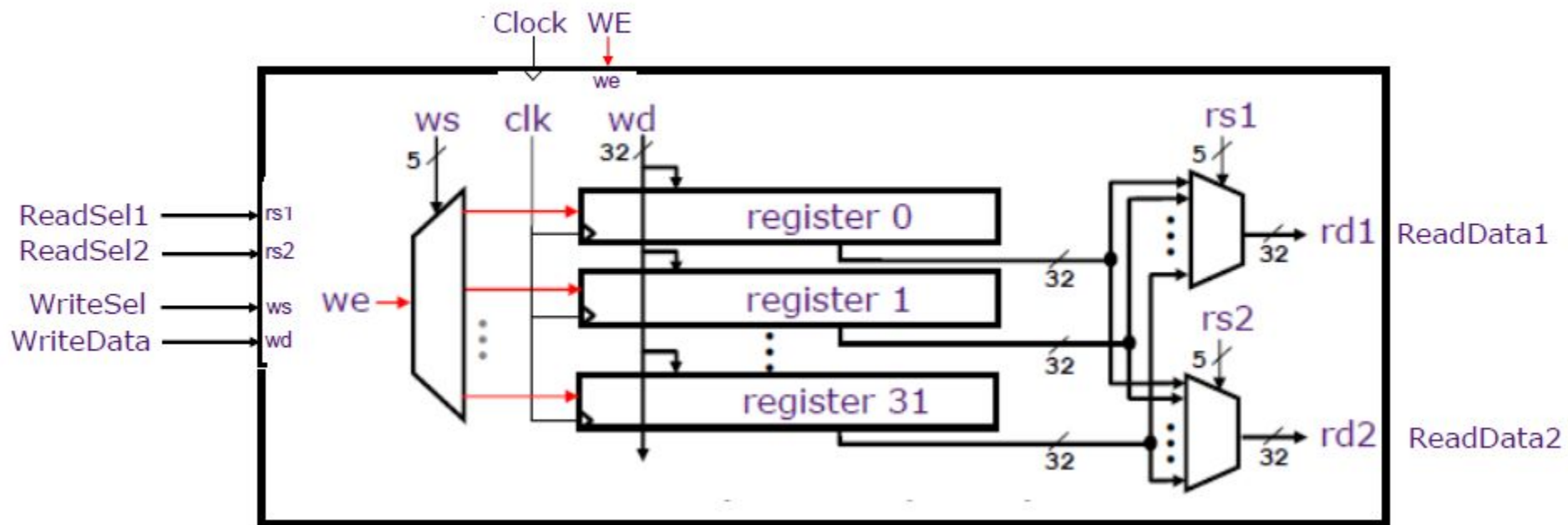- No timing issues in reading a selected register
- Register files with a large number of ports are difficult to design
  - Intel's Itanium, GPR File has 128 registers with 8 read ports and 4 write ports!!!






# Design Register Architecture:

$2R + 1W$

1st operand:  $R_0 - R_7$

2nd " :  $R_8 - R_{15}$

Result field:  $R_{16} - R_{23}$

 



# Instruction Execution



---

Execution of an instruction involves

1. instruction fetch
2. decode and register fetch
3. ALU operation
4. memory operation (optional)
5. write back



and the computation of the address of the *next instruction*

Opcode	R1 (data-1)	R2(data-2)	R3(result)
--------	-------------	------------	------------

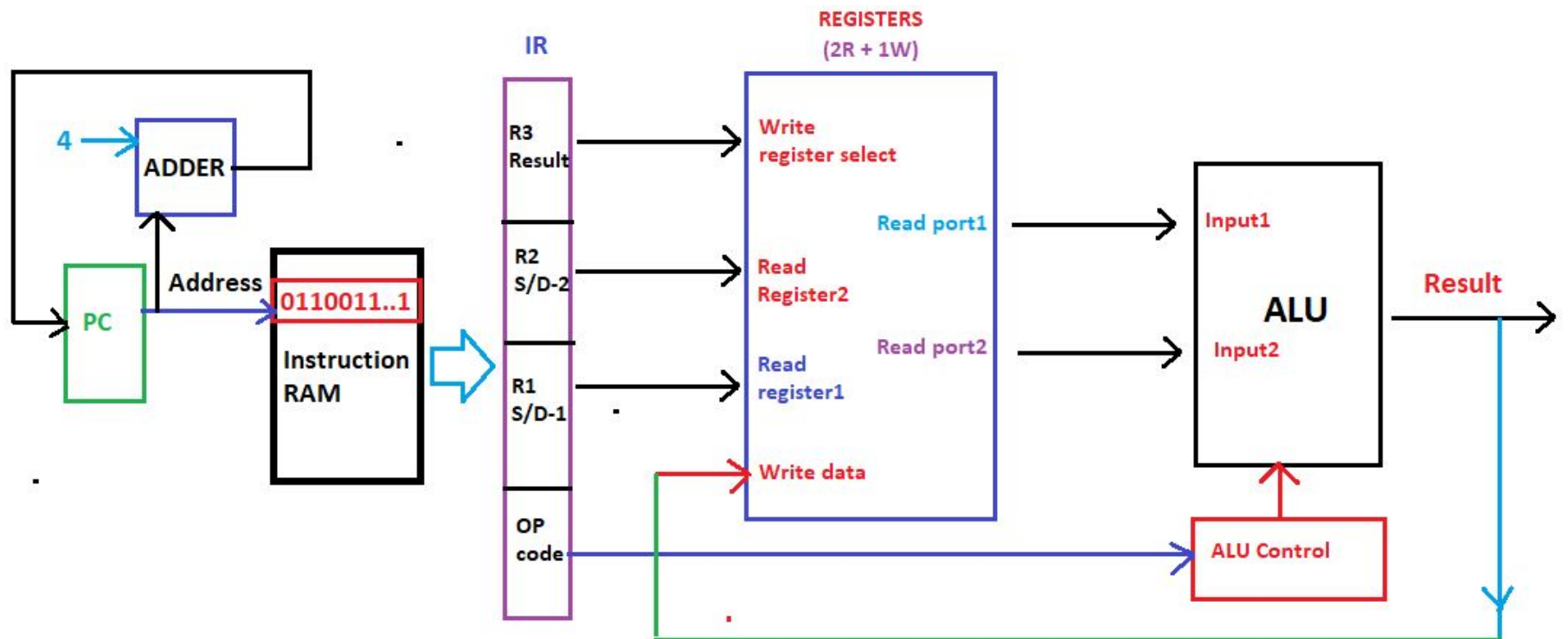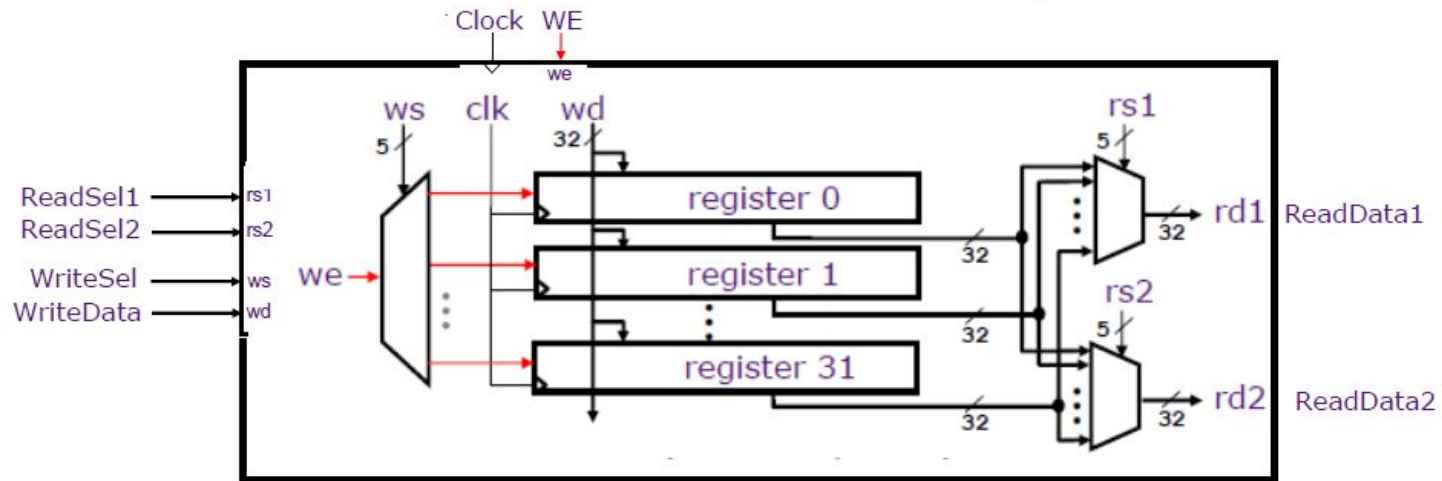


# Register Mode



Opcode	R1 (data-1)	R2(data-2)	R3(result)
--------	-------------	------------	------------

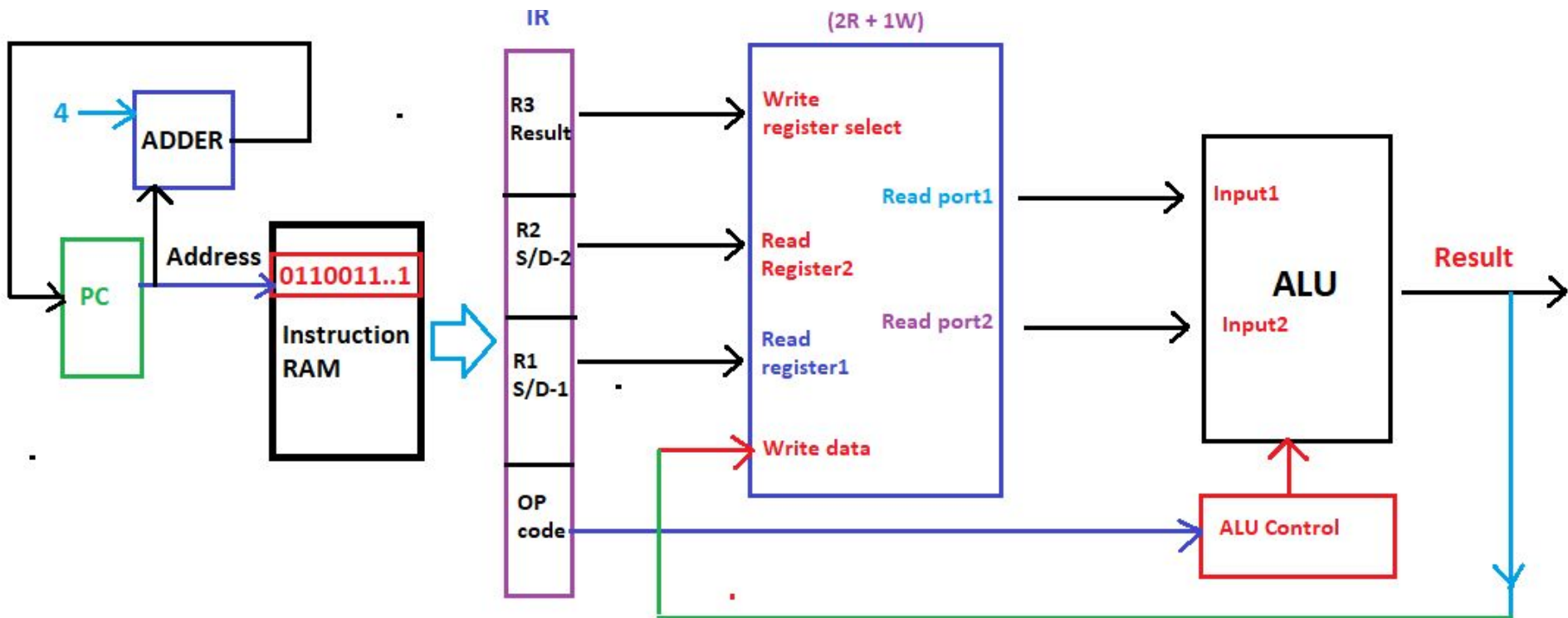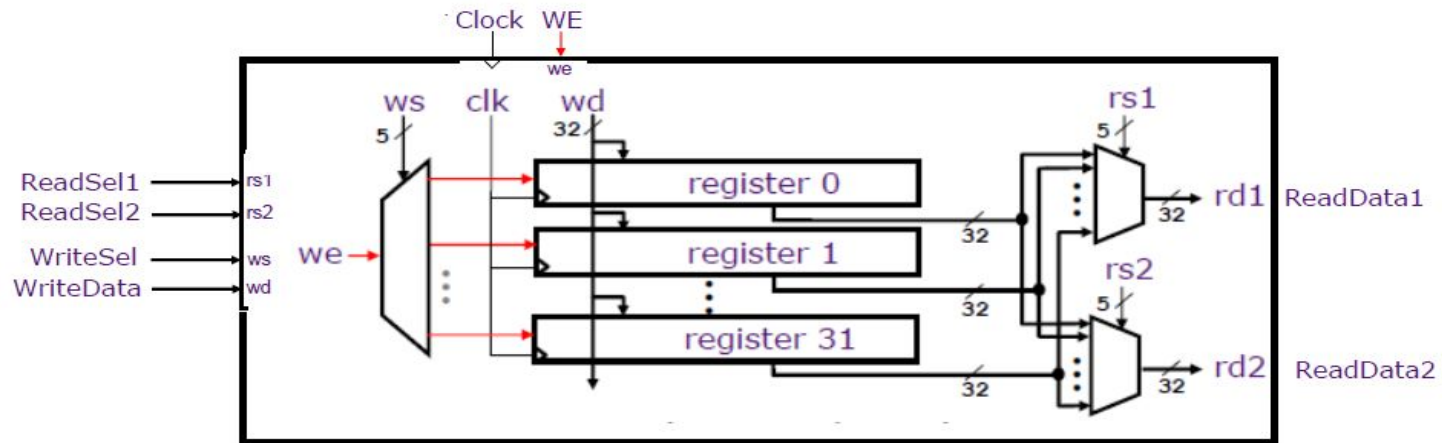


ADD	R1	R2	R3
100001	00001	00010	00011

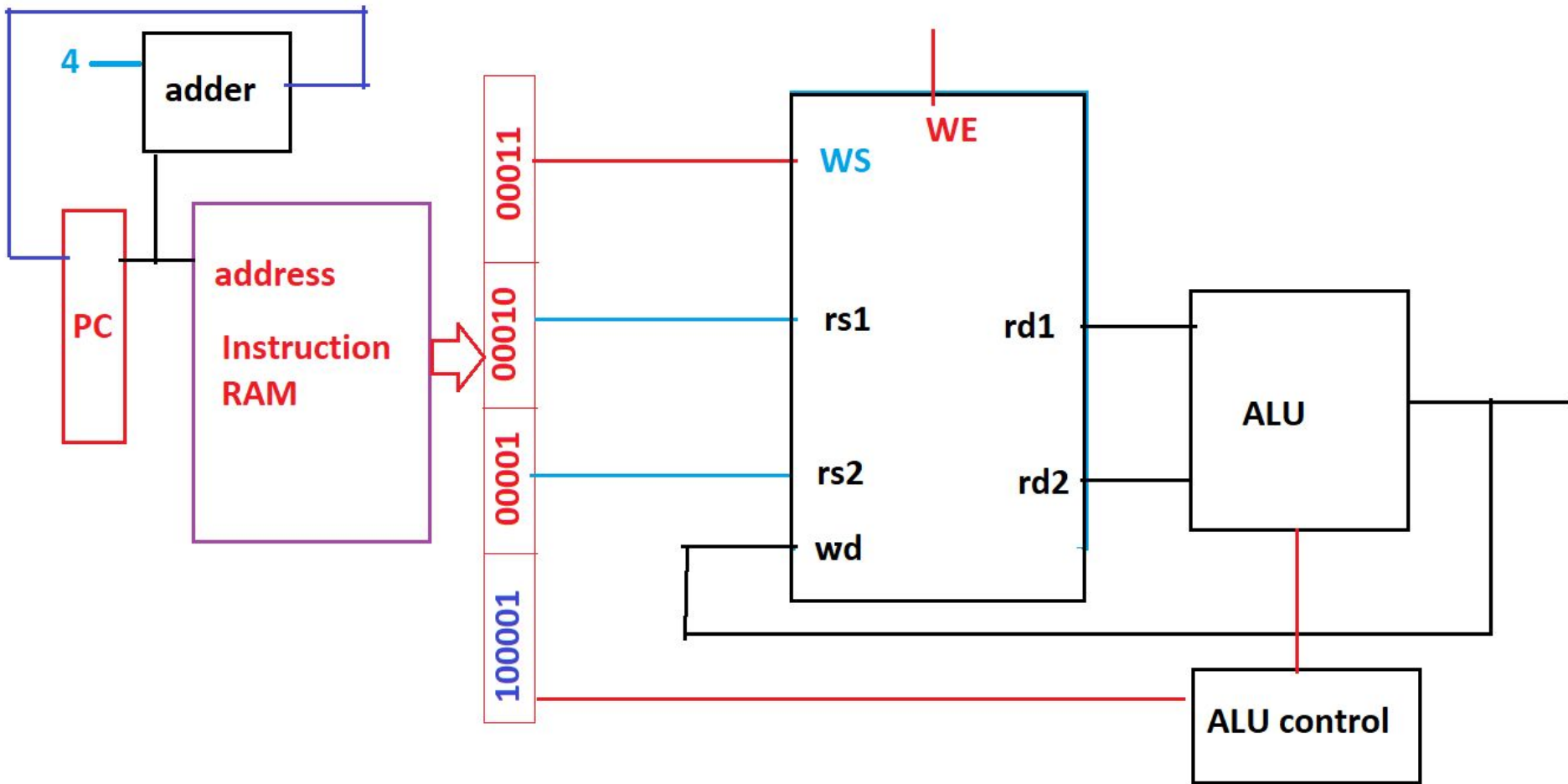

Immediate Mode

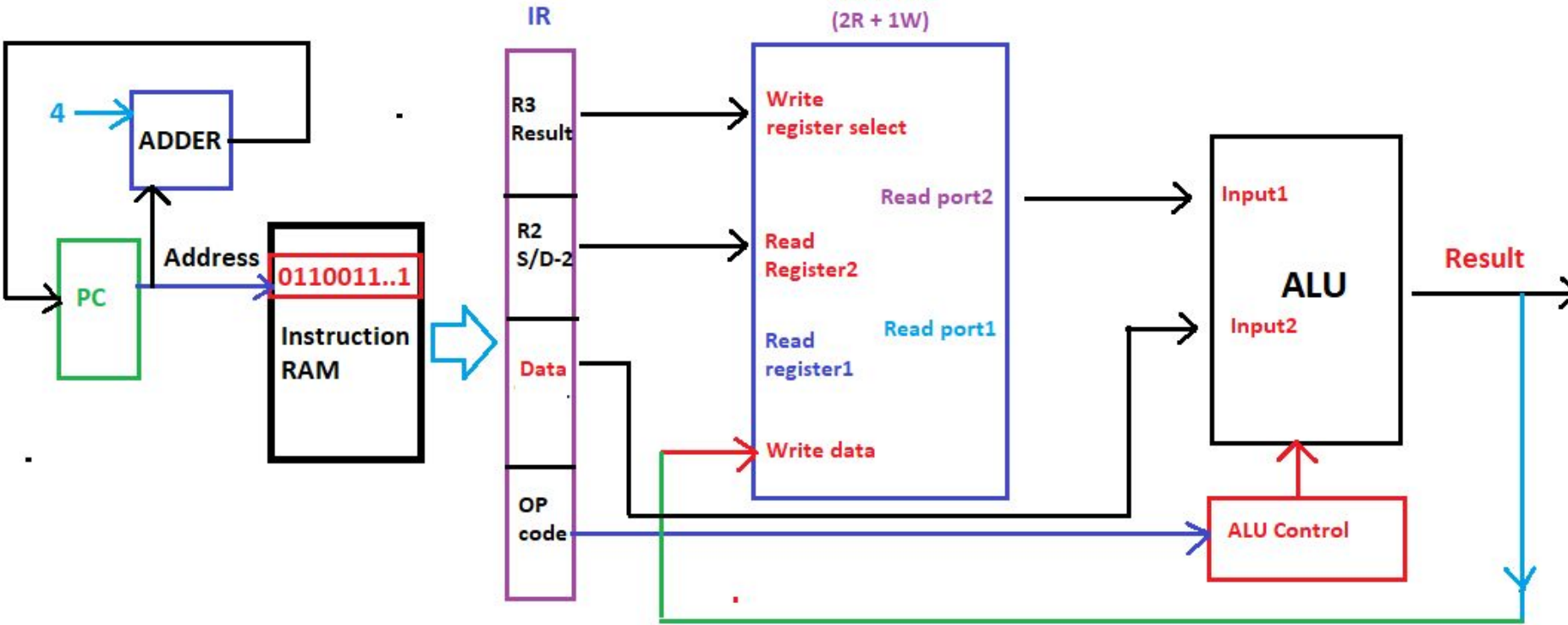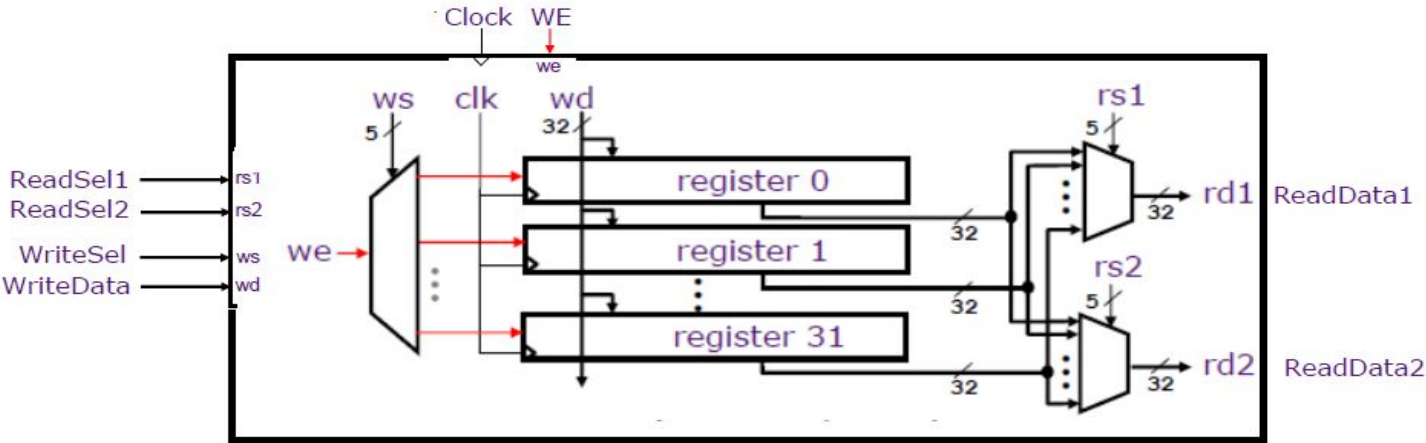




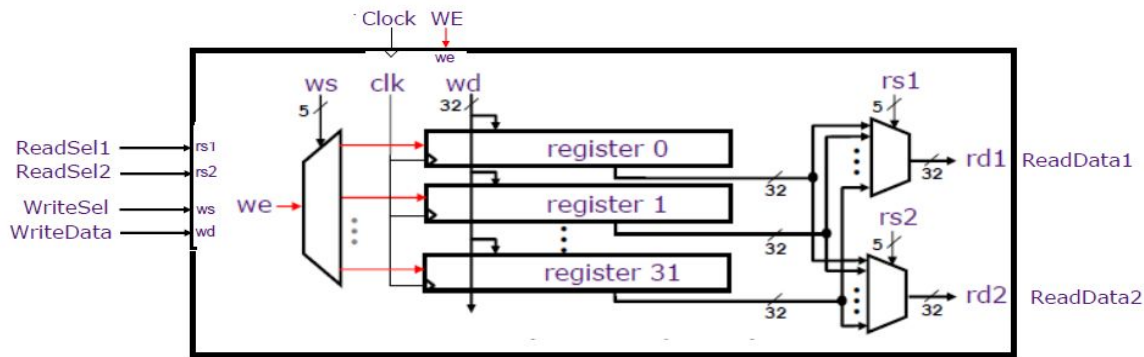

Opcode	R1 (data-1)	R2(data-2)	R3(result)
--------	-------------	------------	------------


Opcode	data-1	R2(data-2)	R3(result)
--------	--------	------------	------------

Immediate Mode & Register Mode

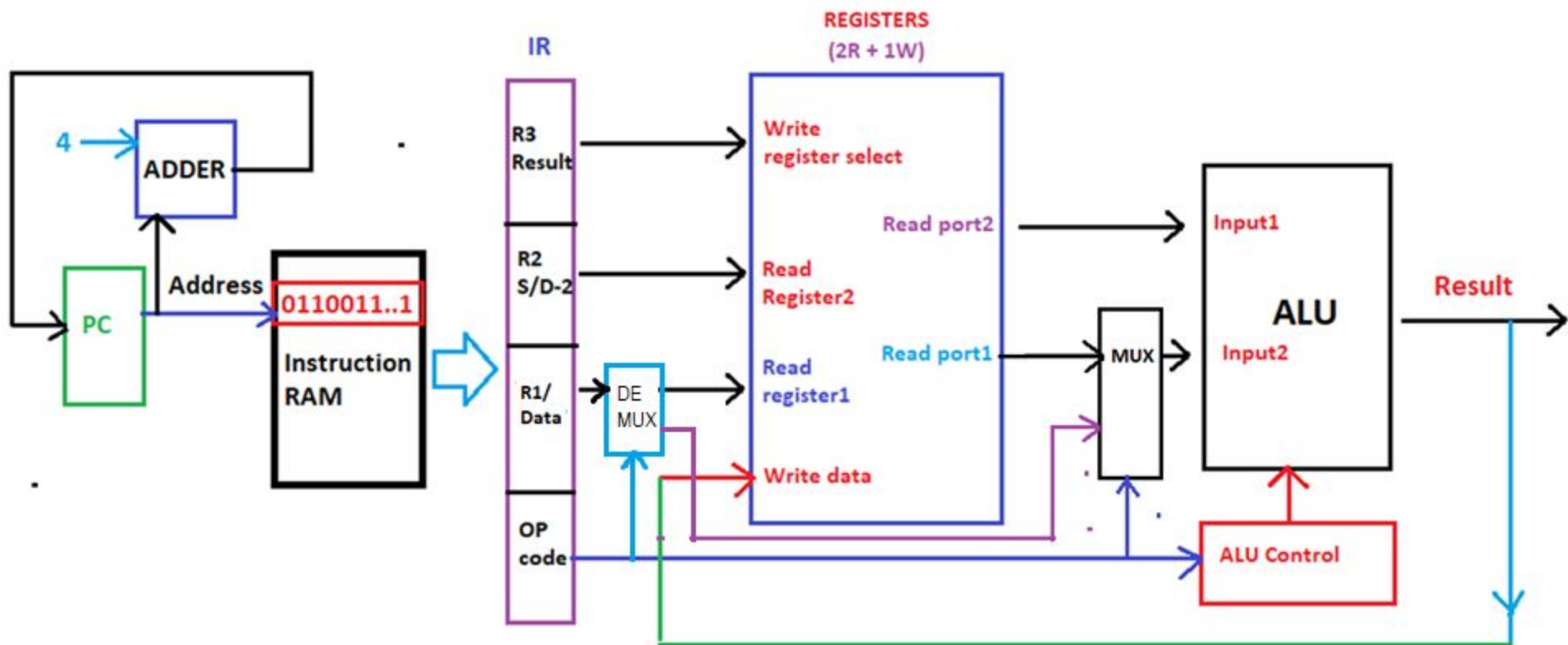

## Memory Indirect mode

LOAD	R1(destination)	R2(base)	124(offset)
------	-----------------	----------	-------------

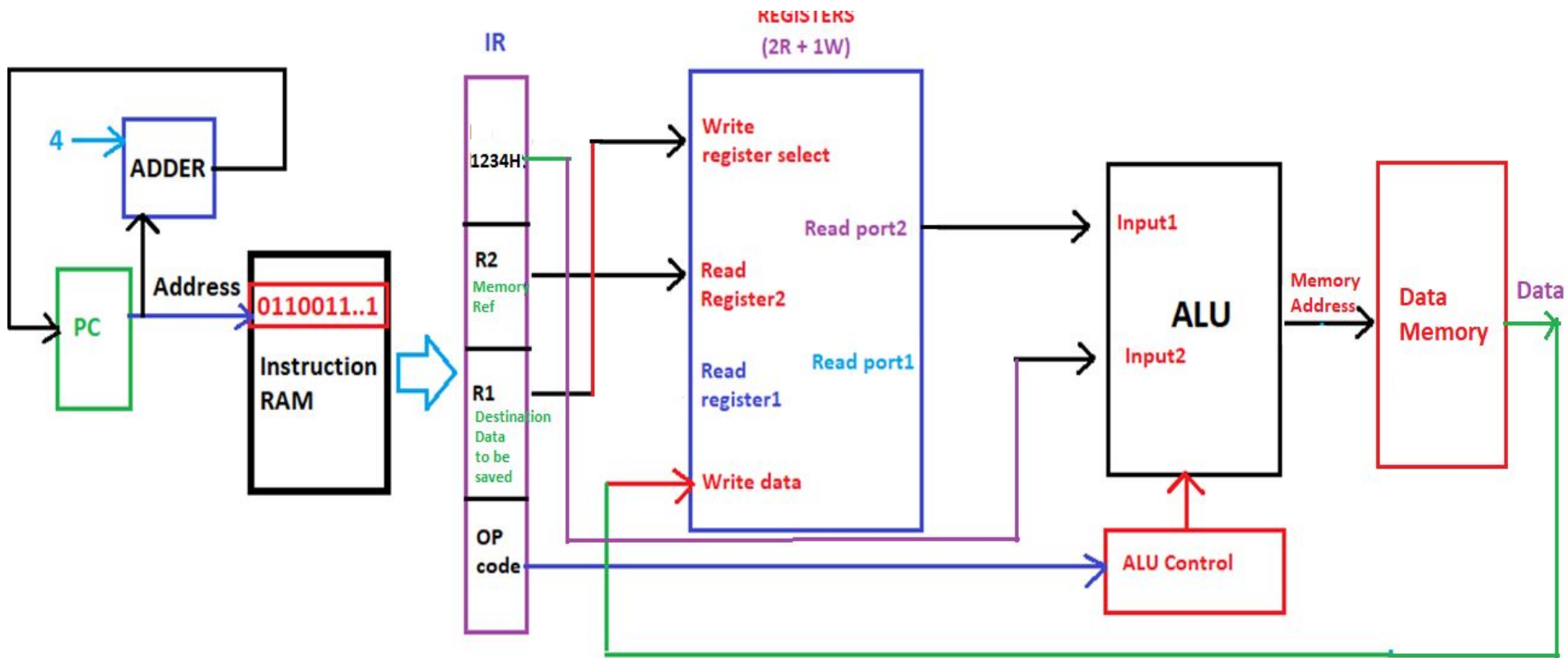

STORE	R1 (source)	R2(base)	124(offset)
-------	-------------	----------	-------------

